

# Management and analysis of physics datasets, Part. 1

Nith Laboratory

---

Antonio Bergnoli [bergnoli@pd.infn.it](mailto:bergnoli@pd.infn.it) - Filippo Marini [filippo.marini@pd.infn.it](mailto:filippo.marini@pd.infn.it)

22/12/2020

## Laboratory Introduction

---

- Build the UART transmitter unit
- Build the UART receiver unit

## Uart Trasmitter

---

 


Figure 1: UART transmitter waveform

# Baudrate Generator

- it is basically a counter
- it has only one output
- output is equal to '1' for exactly one clock cycle every *bit time* ( $T_{bit}$ )

BOARD clock frequency = 100 Mhz ( 10 ns period)

BAUDRATE = 115200 (bit/s)

DIVIDER=  $100.000.000 / 115200 = 868.055$

 


Figure 2: The Baudrate generator

# The Uart Transmitter

 


Figure 3: The Uart Transmitter

# The Uart Transmitter State machine

 


Figure 4: tx State machine idea

The BAUDRATE out signal make possible to switch from a state to another






## Uart Receiver

---
   
# How to retrieve the incoming UART transmission?

The bits are recovered by sampling at the best sampling point: the middle of the baudrate period

Transmit Character 'a' ( ASCII CODE hexadecimal: 61, binary: 01100001) at 115200 Bit/second, no parity bit




$$T_{\text{bit}} = 1/115200 \text{ s} = 8,68 \text{ us}$$
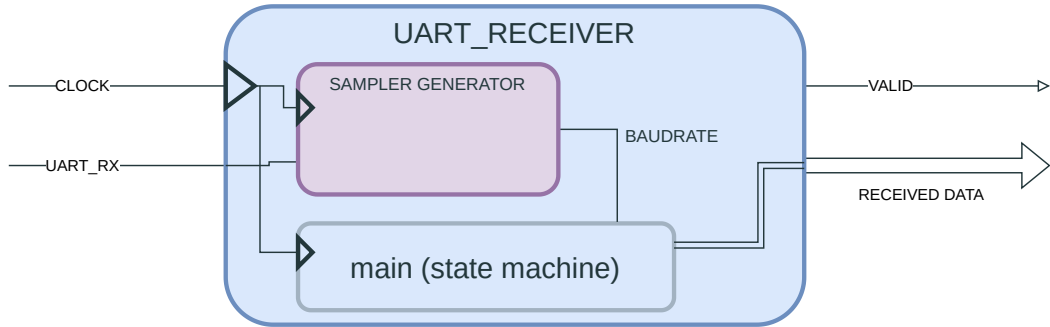
## Modules for the Uart receiver

The UART receiver consists of two main modules:

- The sampler generator
- the main state machine module




The Sampler Generator module is needed to provide the main UART receiver module with the data sampling pulses. Like the transmitter needed the Baudrate generator to transmit the UART bits, now the pulse generator does the same thing, but the pulses are now needed to sample the incoming bits.
 
# The Sampler Generator

Just like the UART transmitter main module, the sampler generator is made up of 3 different submodules:


- The pulse generator
- The state machine
- the delay line


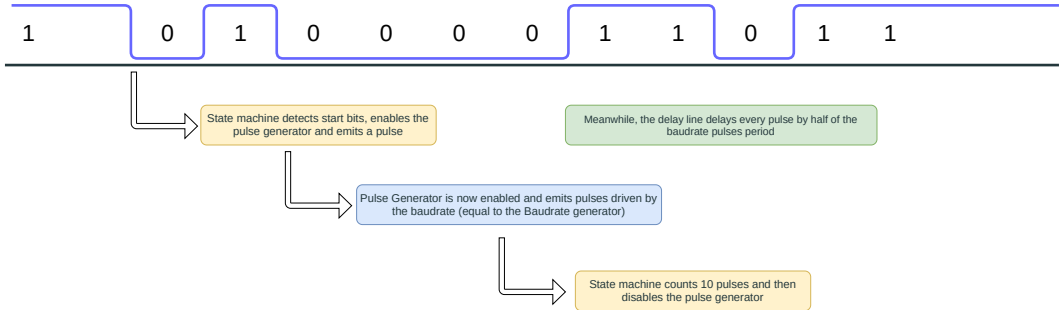
# What does the Sampler Generator do?

The behaviour of the sampler generator is the following:

Transmit Character 'a' ( ASCII CODE hexadecimal: 61, binary: 01100001) at 115200 Bit/second, no parity bit



- Design the Sampler Generator module and simulate it
- Design the UART Receiver module and simulate it